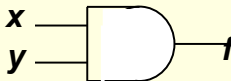
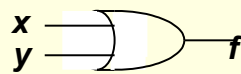
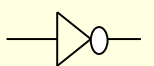


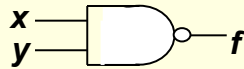
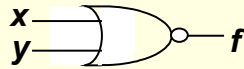
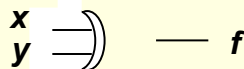

LOGIC GATES AND BOOLEAN ALGEBRA

CHAPTER 2 (CONT.....)

Logic Gates

Name	Graphical Symbol	Algebraic Function	Truth Table															
AND		$f = x.y$	<table><tr><th>x</th><th>y</th><th>f</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	f	0	0	0	0	1	0	1	0	0	1	1	1
x	y	f																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$f = x + y$	<table><tr><th>x</th><th>y</th><th>f</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	f	0	0	0	0	1	1	1	0	1	1	1	1
x	y	f																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
INVERTER		$f = x'$	<table><tr><th>x</th><th>f</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	f	0	1	1	0									
x	f																	
0	1																	
1	0																	

Logic Gates

Name	Graphical Symbol	Algebraic Function	Truth Table															
NAND		$f = (x.y)'$	<table><tr><th>x</th><th>y</th><th>f</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	f	0	0	1	0	1	1	1	0	1	1	1	0
x	y	f																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$f = (x + y)'$	<table><tr><th>x</th><th>y</th><th>f</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	f	0	0	1	0	1	0	1	0	0	1	1	0
x	y	f																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
EX-OR		$f = x'y + xy'$	<table><tr><th>x</th><th>y</th><th>f</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	f	0	0	0	0	1	1	1	0	1	1	1	0
x	y	f																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
EX-NOR		$f = x'y' + xy$	<table><tr><th>x</th><th>y</th><th>f</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	f	0	0	1	0	1	0	1	0	0	1	1	1
x	y	f																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

Boolean Expression

- Boolean expressions are a much better form for representing digital circuits because it is much easier to manipulate and simplify.
- A Boolean expression is an expression formed with:
 - binary variables
 - the binary operators **OR** and **AND**
 - the operator **NOT**
 - parentheses
 - an equal sign
- For example,
 - $F = \overline{x}y + z$ **F** is **1** when $z = 1$ **OR** when $x = 0$ **AND** $y = 1$.
- The precedence of operations is as follows:
 - parentheses,
 - NOT,
 - AND
 - OR.

Boolean Algebra


- **Definition:** Theorems that are used at design time to manipulate and simplify Boolean expressions for easier and less expensive implementation.
- Any Boolean expression can be represented using only **AND**, **OR**, and **NOT** operations.
- May need to use Boolean algebra to change the form of a Boolean expression to better utilize the types of gates provided by the component library being used.
- A Boolean variable, x , can have two values, typically 1 and 0 (on and off)

Laws and Rules Boolean Algebra



Boolean Addition: <ul style="list-style-type: none"> * $A+0 = A$ * $A+1 = 1$ * $A+A = A$ * $A+\bar{A} = 1$ 	Boolean Multiplication: <ul style="list-style-type: none"> * $A \cdot 0 = 0$ * $A \cdot 1 = A$ * $A \cdot A = A$ * $A \cdot \bar{A} = 0$
Complement Rules: <ul style="list-style-type: none"> * $A = \overline{\overline{A}}$ * $A = A$ 	Boolean other Rules: <ul style="list-style-type: none"> * $A+AB = A$ * $A+\bar{A}B = A+B$ * $\bar{A}+AB = \bar{A}+B$
Commutative Laws: <ul style="list-style-type: none"> $A+B = B+A$ $A \cdot B = B \cdot A$ 	Associative Laws: <ul style="list-style-type: none"> $A+(B+C) = (A+B)+C$ $A(BC) = (AB)C$
Distributive Laws: <ul style="list-style-type: none"> $A(B+C) = AB+AC$ * $(A+B)(A+C) = A+BC$ 	Demorgan's Theorem: <ul style="list-style-type: none"> $\overline{XY} = \bar{X} + \bar{Y}$ $\overline{X+Y} = \bar{X}\bar{Y}$

Boolean Analysis of Logic Circuits

 - The Boolean Expression for a Logic Circuit
 - Any logic circuit, may completely described using the Boolean expressions.
 - To derive the Boolean Expression of a given logic circuit, begin the left-most inputs and work toward the final output, writing the expression for each gate.
 - Ex:



Boolean Analysis of Logic Circuits

  

Boolean Analysis of Logic Circuits

- Constructing Truth Table for a logic circuit
 - Once the Boolean expression has been determined, truth table can be developed.
 - Boolean expression have to evaluate for all possible combinations of values input variable.
 - If there are four input variables (A, B, C, D) therefore sixteen ($2^4=16$) combinations of values possible.
- Evaluating the Expression:
 - To evaluate the expression, first find the values of the variables that make the expression equal to 1, using rules for Boolean addition and multiplication.

Boolean Analysis of Logic Circuits

- Putting the Results in Truth Table Format.
 - The first step, list the sixteen input variable combinations of 1s and 0s in binary sequence.
 - Place a 1 in the output column for each combination of input variables.
 - Place a 0 in the output column for all other combinations input variables.

DeMorgan's Theorem

- Apply DeMorgan's theorem to the expression:

- \overline{WXYZ}

- $\overline{W + X + Y + Z}$

- $\overline{(A + B + C)D}$

- $\overline{A\bar{B} + \bar{C}D + EF}$

Simplification Using Boolean Algebra

■ Ex: Simplify the Boolean expression

■
$$Y = AB + A(B + C) + B(B + C)$$

■
$$F = (X + Y)(X + \bar{Y})(\bar{X} + Z)$$

■
$$[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$$

■
$$\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$$

■
$$\overline{AB + AC} + \bar{A}\bar{B}C$$

■
$$F = XY + \bar{X}Z + YZ$$

Standard Forms of Boolean Expressions

- All Boolean expressions, regardless of their form can be converted into either of two standard forms:
 - sum-of-product forms
 - product-of-sums forms
- Standardization makes the evaluation, simplification and implementation of Boolean expressions much more systematic and easier.

Standard Forms of Boolean Expressions

- Sum-of-products (SOP) form:
 - Two or more product terms are summed by Boolean addition.
 - OR the outputs of two or more AND gates.
 - Eg: $\overline{A}BC + \overline{A}\overline{B} + A\overline{B}\overline{C}D$
 - A single over bar cannot extend over more than one variable, eg: \overline{ABC}
 - Standard SOP-all the variables in the domain appear in each product term, eg: $\overline{A}\overline{B}CD + \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D$

Sum-of-products (SOP)

- Converting product terms to standard SOP
 - Step 1: multiply each nonstandard product term by a term made up of the sum of a missing variable and its complement.
 - Repeat step 1 until all resulting product terms contain all variables.
 - Ex: Convert following Boolean expression into standard SOP form: $\overline{A}\overline{B}C + \overline{A}\overline{B} + A\overline{B}\overline{C}D$

Standard Forms of Boolean Expressions

- Product-of-Sums (POS) form:
 - Two or more sum terms are multiplied by Boolean multiplication.
 - AND the outputs of two or more OR gates.
 - Eg: $(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$
 - A single over bar cannot extend over more than one variable, eg: $\overline{A + B + C}$
 - Standard POS- all the variables in the domain appear in each product term, eg: $(A + B + \bar{C} + D)(A + \bar{B} + \bar{C} + \bar{D})(\bar{A} + B + C + \bar{D})$

Product-of-Sums (POS)

- Converting a sum term to Standard POS
 - Add to each nonstandard product term a term made up of the product of the missing variable and its complement.
 - Repeat step 1 until all resulting sum terms contain all variables.
 - Ex: Convert the following Boolean expression into standard POS form: $(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$

Standard Forms of Boolean Expressions

- Converting Standard SOP to Standard POS
 - Step1: Determine the binary numbers for each literal.
 - Step2: Determine the absent binary numbers.
 - Step3: Write the binary numbers from Step 2 in equivalent term in opposite standard
- Ex: Convert the following SOP expression to an equivalent POS expression

$$\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC$$

Converting Standard SOP & Standard POS to Truth Table Format

- SOP- equal to 1 only if at least one of the product terms is equal to 1.
- POS-equal to 0 only if at least one of the sum terms is equal to 0.


Converting Standard SOP to Truth Table Format

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$\overline{\overline{A}}\overline{B}C$

$\overline{A}BC$

$A\overline{B}C$

 

- Ex: Develop the truth table for the expression $Y = \overline{\overline{A}}\overline{B}C + \overline{A}BC$ and draw the logic circuit.


Converting Standard POS to Truth Table Format

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$A + \bar{B} + C$$

$$\bar{A} + B + C$$

$$\bar{A} + \bar{B} + \bar{C}$$

 

- Ex: Develop the truth table for $(A + \bar{B}) \cdot (\bar{A} + B) \cdot (A + B)$ and draw logic circuit.

The Karnaugh Map (K-map)

- Is an array of cells in which each cell represents a binary value of the input variables.
- Can be used for expressing two, three, four, and five variables.
- Mapping a nonstandard SOP expression:
 - A Boolean expression must first be in standard form before putting in Karnaugh map.

The K-Map SOP Minimization

- Grouping/looping the 1s
 - Each cell in a group must be adjacent, this included wrap-around adjacent.
 - Maximize the size of the groups, but minimize the number of groups.
 - A group must contain either 1,2,4,16 cells (power of 2).
 - Overlapping groups is allowed.
- Determine the minimum SOP expression
 - Each group of cells containing 1s creates one product terms composed of all variables that occur either uncomplemented or complemented.
 - Variables with both uncompleted and complemented within the group are eliminated.

2 variables K-map

- A two variable K-map with their truth table which is showing product terms of each line as shown below

A	B	Product term
0	0	$\overline{A}\overline{B}$
0	1	$\overline{A}B$
1	0	$A\overline{B}$
1	1	AB

	B	B
\overline{A}	$\overline{A}\overline{B}$	$\overline{A}B$
A	$A\overline{B}$	AB

- Ex: Map the following SOP expression of two variables. $\overline{A}\overline{B} + A\overline{B} + AB$

2 variables K-map

A	B	X
0	0	1 → $\bar{A}\bar{B}$
0	1	0
1	0	0
1	1	1 → AB

$$\left\{ x = \bar{A}\bar{B} + AB \right\}$$

	\bar{B}	B
\bar{A}	1	0
A	0	1

(a)

3 Variable K-map

A	B	C	Product terms
0	0	0	$\overline{A}\overline{B}\overline{C}$
0	0	1	$\overline{A}\overline{B}C$
0	1	0	$\overline{A}B\overline{C}$
0	1	1	$\overline{A}BC$
1	0	0	$A\overline{B}\overline{C}$
1	0	1	$A\overline{B}C$
1	1	0	$AB\overline{C}$
1	1	1	ABC

	\overline{C}	C
$\overline{A}\overline{B}$	$\overline{A}\overline{B}\overline{C}$	$\overline{A}\overline{B}C$
$\overline{A}B$	$\overline{A}B\overline{C}$	$\overline{A}BC$
$A\overline{B}$	$A\overline{B}\overline{C}$	$A\overline{B}C$
AB	$AB\overline{C}$	ABC

- Ex: Map the SOP expression $\overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}C + ABC$ of three variables.

3 Variable K-map

A	B	C	X
0	0	0	1 → $\bar{A}\bar{B}\bar{C}$
0	0	1	1 → $\bar{A}\bar{B}C$
0	1	0	1 → $\bar{A}B\bar{C}$
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1 → $AB\bar{C}$
1	1	1	0

$$\left\{ \begin{aligned} X = & \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C \\ & + \bar{A}B\bar{C} + AB\bar{C} \end{aligned} \right\}$$

(b)

	\bar{C}	C
$\bar{A}\bar{B}$	1	1
$\bar{A}B$	1	0
AB	1	0
$A\bar{B}$	0	0

4 Variable K-map

A	B	C	D	X
0	0	0	0	0
0	0	0	1	1 → $\bar{A}\bar{B}\bar{C}D$
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1 → $\bar{A}B\bar{C}D$
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1 → $AB\bar{C}D$
1	1	1	0	0
1	1	1	1	1 → $ABCD$

$$\left\{ \begin{aligned} X = & \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D \\ & + AB\bar{C}D + ABCD \end{aligned} \right\}$$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	0	0
$\bar{A}B$	0	1	0	0
AB	0	1	1	0
$A\bar{B}$	0	0	0	0

(c)

4 Variable K-map

- Ex: Map the following four variable SOP expressions:

$$\overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + A\overline{B}C\overline{D} + A\overline{B}CD + ABC\overline{D} + ABCD$$

More examples

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0 1	0 2	0 3	1 4
$\bar{A}B$	0 5	1 6	1 7	0 8
AB	0 9	1 10	1 11	0 12
$A\bar{B}$	0 13	0 14	1 15	0 16

$$X = \underbrace{\bar{A}\bar{B}C\bar{D}}_{\text{loop 4}} + \underbrace{ACD}_{\text{loop 11, 15}} + \underbrace{BD}_{\text{loop 6, 7, 10, 11}}$$

(a)

More examples

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0 1	0 2	1 3	0 4
$\bar{A}B$	1 5	1 6	1 7	1 8
AB	1 9	1 10	0 11	0 12
$A\bar{B}$	0 13	0 14	0 15	0 16

$$X = \underbrace{\bar{A}B}_{\text{loop 5, 6, 7, 8}} + \underbrace{B\bar{C}}_{\text{loop 5, 6, 9, 10}} + \underbrace{\bar{A}CD}_{\text{loop 3, 7}}$$

(b)

More examples

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0 1	1 2	0 3	0 4
$\bar{A}B$	0 5	1 6	1 7	1 8
AB	1 9	1 10	1 11	0 12
$A\bar{B}$	0 13	0 14	1 15	0 16

$$X = \underbrace{ABC}_{9, 10} + \underbrace{\bar{A}\bar{C}D}_{2, 6} + \underbrace{\bar{A}BC}_{7, 8} + \underbrace{ACD}_{11, 15}$$

(c)

More examples

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	0	0
$\bar{A}B$	0	1	1	1
AB	0	0	0	1
$A\bar{B}$	1	1	0	1

$$X = \bar{A}\bar{C}D + \bar{A}BC + A\bar{B}\bar{C} + ACD\bar{D}$$

(a)

More examples

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	0	0
$\bar{A}B$	0	1	1	1
AB	0	0	0	1
$A\bar{B}$	1	1	0	1


$$X = \bar{A}BD + BCD + \bar{B}\bar{C}D + A\bar{B}\bar{D}$$

(b)

More examples

- Use a K-map to simplify the following Boolean function:

$$F(A,B,C) = \sum m(0,2,3,7)$$

 

More examples

- Use a K-map to simplify the following Boolean function:

$$F(A,B,C,D) = \prod M(0,1,2,4,9,11,15)$$

$$F(A,B,C,D) = \sum m(3,5,6,7,8,10,12,13,14)$$

AB \ CD	CD			
	00	01	11	10
00	0	1	1	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Prime Implicants

AB \ CD	CD			
	00	01	11	10
00	0	1	1	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Essential Prime Implicants

AB \ CD	CD			
	00	01	11	10
00	0	1	1	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Final Expression

$$F(A,B,C,D) = BC'D + AD' + A'CD + BCD'$$

“Don’t Care” On Karnaugh Map

- “Don’t Care” conditions
 - Eg: in BCD code which have 6 invalid combination: 1010, 1011, 1100, 1101, 1110, and 1111.
 - A “X” is placed in the cell.
 - It can be treat as either 1 or 0.
 - When grouping, the Xs, it can be treated as 1s to make a larger grouping.

The K-Map POS Minimization

- Determine the minimum SOP expression
 - Determine the binary value of each sum term in the standard POS expression.
 - As each sum term is evaluated, place a 0 on the Karnaugh map in the corresponding cell.

The K-Map POS Minimization

- Ex: Map the following standard POS expression on a K-map.

$$1) \quad (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C)$$

$$2) \quad (\bar{A} + \bar{B} + C + D)(\bar{A} + B + \bar{C} + \bar{D})(A + B + \bar{C} + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D})(A + B + \bar{C} + \bar{D})$$